

# LADDER LOGIC 2

## 🤖 Chapter 5-2: Basic Instructions in Ladder Logic

### Boolean Logic and the DNA of Control

Now that you know what Ladder Logic looks like, it's time to understand **how it actually decides things**. And that takes us straight into **Boolean logic** — the bedrock of all decision-making in PLCs.


Don't worry, this isn't Digital Systems 101 — we're not breaking out Karnaugh maps or Boolean algebra proofs. We're just gonna look at the essentials: **AND** and **OR** logic.

### ❏ Boolean Logic in Plain Language

PLC logic is built on simple True/False decisions — like light switches:

- **TRUE (1)** → There's voltage or a condition is satisfied
- **FALSE (0)** → No voltage or the condition isn't satisfied

 
From this binary setup, we build logic gates. In Ladder Logic, these gates are **not separate components** — they're created through **how you arrange your rungs and contacts**.



## The Gates — Series Logic

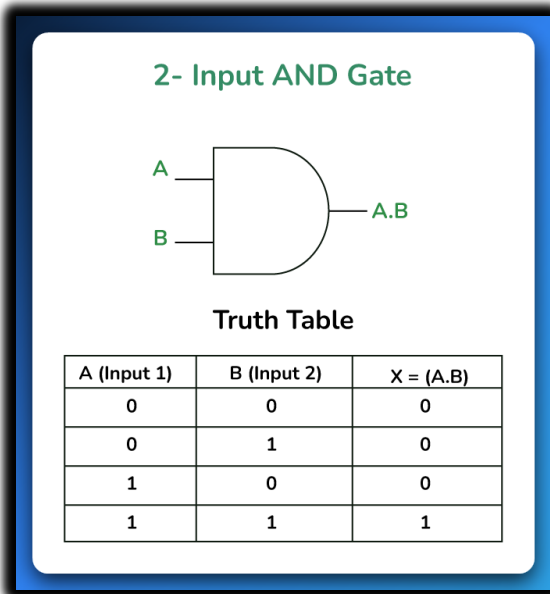
### 🔑 AND gate Ladder Implementation:

AND operations are analogous to **multiplication**.



Use **normally open contacts** in series.

This is saying:

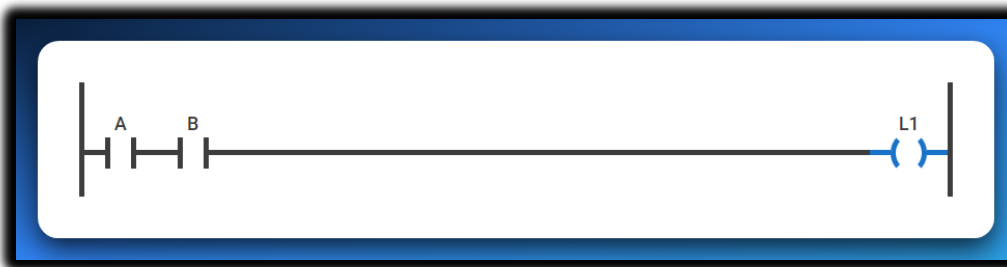

*"Only if A **AND** B are both TRUE, then turn ON the output."*


If either A or B is FALSE, current stops flowing — just like if one switch in a series circuit is off.

$$A \cdot B = X$$
 
## **OR gate Ladder Implementation:**

Use **normally open contacts in parallel**.


**OR** operations are comparable to **addition**.



This is saying:

*"If A **OR** B is TRUE, then turn ON the output."*

 As long as at least one of them is ON, the rung is complete and current flows to the output.




If **A is TRUE** (and B is FALSE), the path through A "closes," allowing logical power to flow to the output.



If **B is TRUE** (and A is FALSE), the path through B "closes," allowing logical power to flow to the output.

If **both A and B are TRUE**, both paths "close," and logical power still flows to the output.

 Only if **both A and B are FALSE** will both paths remain "open," stopping the logical power flow and keeping the output OFF.



## 🔑 XOR gate Ladder Implementation:

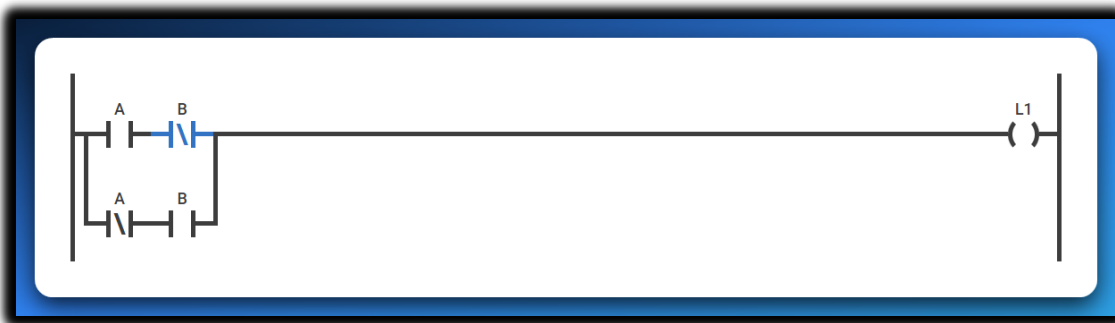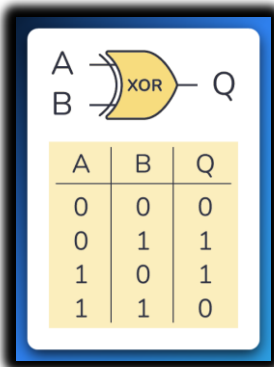

Use a combination of normally open (NO) and normally closed (NC) contacts.  
This represents the logic: **"If A OR B is TRUE, but not both, then turn ON the output."**

### How it works:

- **If A is TRUE and B is FALSE:**  
The path through A (NO) and B (NC) closes → Output turns ON.
- **If B is TRUE and A is FALSE:**  
The path through B (NO) and A (NC) closes → Output turns ON.
- **If both A and B are TRUE:**  
Both paths are blocked because NC contacts open → Output stays OFF.
- **If both A and B are FALSE:**  
Neither NO contact allows current → Output stays OFF.

✅ **Summary:** Output is ON **only when A or B is TRUE**, but **not both at the same time** — exactly what XOR logic means.

$$(A \cdot \bar{B}) + (\bar{A} \cdot B) = X$$

## 💡 Key Concept: Contacts Are Logic Conditions

In Ladder Logic, your contacts (—| |—) aren't checking voltage directly — they're checking **bit states** in memory.

- A contact in a rung is **like a mini IF-statement**.
- When you place them **in series**, it means “all must be true” (AND).
- When you place them **in parallel**, it means “any can be true” (OR).

And these logic structures determine whether **your output coils (—( )—)** get energized or not.

## 🧠 Analogy Time:

- Think of series logic like **security clearance**:  
“You need both a keycard **and** a password to enter.”
- Think of parallel logic like **alarm triggers**:  
“*If **any** of the sensors trip, sound the alarm.*”

## 📌 Summary:

- **AND Logic = Series contacts** → All must be TRUE.
- **OR Logic = Parallel contacts** → At least one must be TRUE.
- No separate gate components — it's all about **how you arrange your contacts** in the rung.


## The contacts

### 🔑 Normally Open (NO) Contact – The “Push-to-Start”

Think of a normally open contact like a simple doorbell button.

- **Default (not pressed):** The internal path is open. No current flows. In PLC terms, the memory bit is FALSE (0).
- **When pressed:** The path closes. Electricity flows. In PLC terms, the bit flips to TRUE (1), and logical power can now travel through that rung.

 ✅ **Analogy:** Press button → bridge closes → current flows → light turns on.




### 🛡️ Normally Closed (NC) Contact – The “Safety Gate”

Now flip the logic. A normally closed contact is like a safety gate that’s already allowing current through until you interfere.

- **Default (not pressed):** The path is closed. Electricity flows. In PLC terms, the memory bit is TRUE (1).
- **When pressed:** The path opens. Current stops. In PLC terms, the bit reads FALSE (0), blocking logical power on that rung.

 ✅ **Analogy:** Press button → bridge opens → no current → light stays off.




💡 **Bottom line:**

NO let's power through *when active*. NC stops power *when active*.

Together, they're the Lego blocks of ladder logic—defining exactly when your rungs conduct or block logical “power.”

Simple, powerful, and everywhere in your PLC world.

A PLC.

 

By now we're good to go forward with this topic.


# LADDER LOGIC PART 3

## Elements of ladder logic

- **Rails** – Vertical lines that carry electrical power to the control circuit.
- **Rungs** – Horizontal lines where the logic is built; they contain inputs, outputs, and branches.
- **Branches** – Parallel paths on a rung that allow multiple input conditions.
- **Inputs** – Devices like switches or sensors that control the logic flow.
- **Outputs** – Devices like motors or lights activated by the logic.
- **Timer** – Delays actions for a set time (e.g., turn on a light after 5 seconds).
- **Counter** – Counts events or cycles and triggers actions after a set number.

I see a small naming confusion I have always had.

 In my school, we used “Ladder Logic” to refer to the programs we were drawing.



So, I had this conflict calling the **image b** ladder logic.


Now am seeing it being called **relay logic**.

- **Diagram 'a' (Motor Control PLC Ladder Logic):** This is a **program** that runs inside a PLC. It's software.
- **Diagram 'b' (Motor Control Relay Logic):** This is a **wiring diagram** for physical electrical components (relays, switches, motor). It's hardware.




## Some Practice

$$Y = (X1 + X2)X3$$

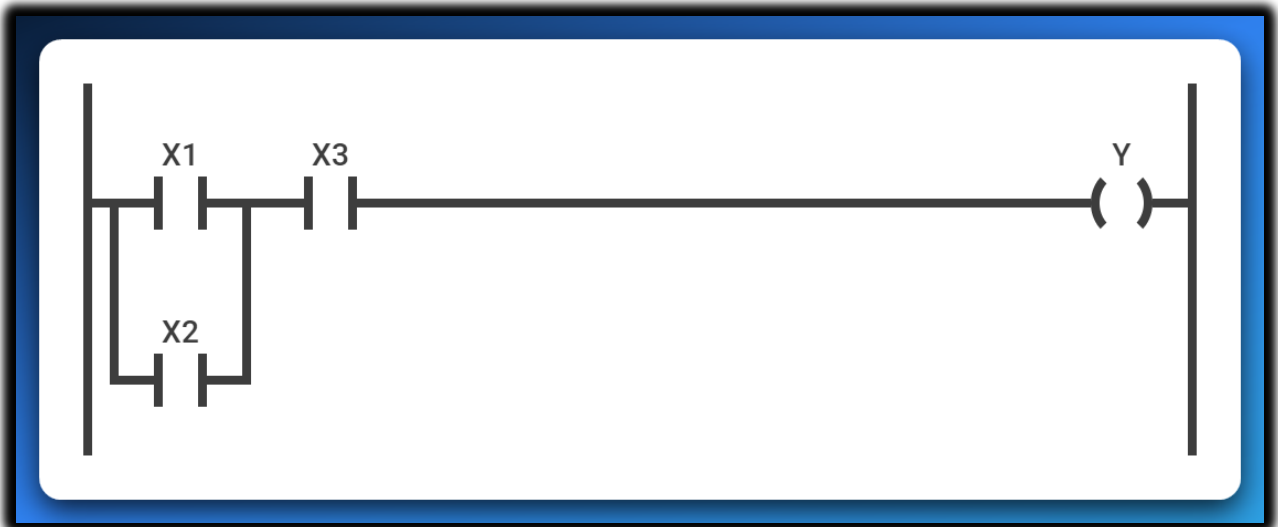



Read it using the AND, OR gates.



$$Y = (X1 + X2)(X3 + X4)$$


 





You could attach the midpoint lines as one, or separate them as above.


$$Y = (X1X2) + X3$$

  

  


  

   


 


IEC 1131-3	Mitsubishi	OMRON	Siemens	Operation	Ladder diagram
LD	LD	LD	A	Load operand into result register	Start a rung with open contacts
LDN	LDI	LD NOT	AN	Load negative operand into result register	Start a rung with closed contacts
AND	AND	AND	A	Boolean AND	A series element with open contacts
ANDN	ANI	AND NOT	AN	Boolean AND with negative operand	A series element with closed contacts
OR	OR	OR	O	Boolean OR	A parallel element with open contacts
ORN	ORI	OR NOT	ON	Boolean OR with negative operand	A parallel element with closed contacts
ST	OUT	OUT	=	Store result register into operand	An output from a rung

 

 
LD X400 (\*Input at address X400\*)  
 AND X401 (\*AND input at address X401\*)  
 OUT Y430 (\*Output to address Y430\*)



 
LD X400 (\*Input at address X400\*)  
 OR X401 (\*OR input at address X401\*)  
 OUT Y430 (\*Output to address Y430\*)



 LDI X400 (\*NOT input at address X400\*)  
 ANI X401 (\*AND NOT input at address X401\*)  
 OUT Y430 (\*Output to address Y430\*)




 LDI X400 (\*NOT input at address X400\*)  
 ORI X401 (\*OR NOT input at address X401\*)  
 OUT Y430 (\*Output to address Y430\*)



(a)

 LD X400 (\*Load input at address X400\*)  
 ANI X401 (\*AND NOT input at address X401\*)  
 LDI X400 (\*Load NOT input at address X401\*)  
 AND X401 (\*AND input at address X401\*)  
 ORB  
 OUT Y430 (\*Output to address Y430\*)



(b)

A( (\*Load the bracketed term\*)  
 A I0.0 (\*Load input at address I0.1\*)  
 AN I0.1 (\*AND input at address I0.1\*)  
 )  
 O( (\*OR the bracketed term\*)  
 AN I0.0 (\*Load NOT input at address I0.0\*)  
 A I0.1 (\*AND input at address I0.1\*)  
 )  
 = Q2.0 (\*Output to address Q2.0\*)

