

LADDER LOGIC 2

🤖 Chapter 5-2: Basic Instructions in Ladder Logic

Boolean Logic and the DNA of Control

Now that you know what Ladder Logic looks like, it's time to understand **how it actually decides things**. And that takes us straight into **Boolean logic** — the bedrock of all decision-making in PLCs.


Don't worry, this isn't Digital Systems 101 — we're not breaking out Karnaugh maps or Boolean algebra proofs. We're just gonna look at the essentials: **AND** and **OR** logic.

❏ Boolean Logic in Plain Language

PLC logic is built on simple True/False decisions — like light switches:

- **TRUE (1)** → There's voltage or a condition is satisfied
- **FALSE (0)** → No voltage or the condition isn't satisfied

 
From this binary setup, we build logic gates. In Ladder Logic, these gates are **not separate components** — they're created through **how you arrange your rungs and contacts**.



The AND Gate — Series Logic

AND operations are analogous to **multiplication**.


2- Input AND Gate

 

Truth Table


A (Input 1)	B (Input 2)	X = (A.B)
0	0	0
0	1	0
1	0	0
1	1	1

 OR operations are comparable to **addition**.




A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

NOR gate(no need to memorize this):

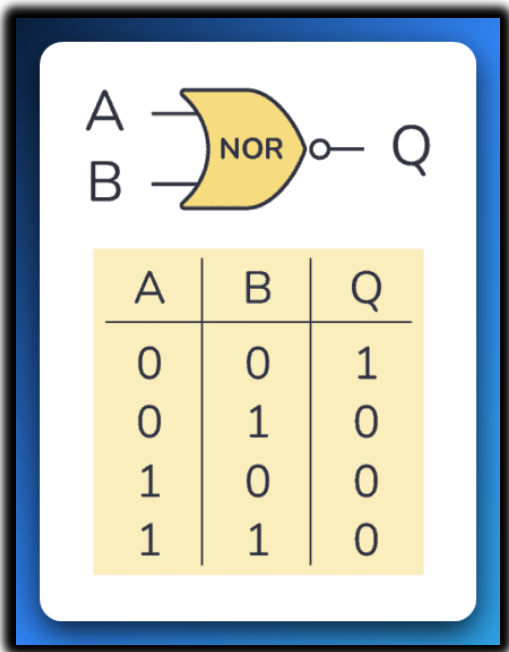

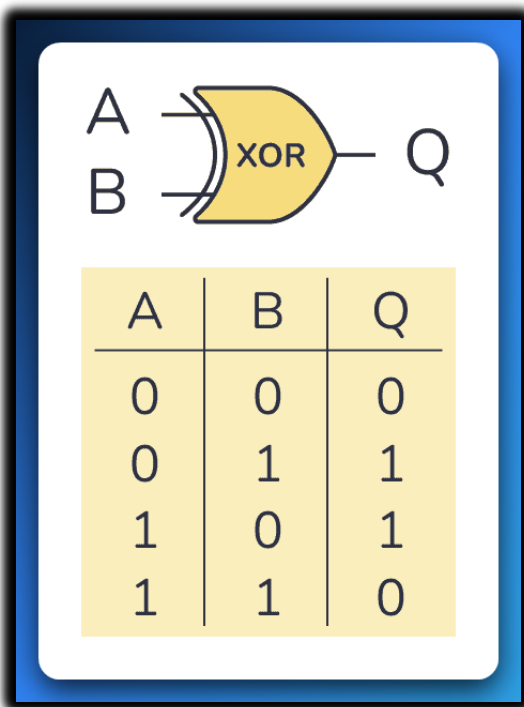
XOR gate(no need to memorize this): A digital logic gate that outputs a "true" (or "1") signal only when an odd number of its inputs are "true" (or "1")



🔑 AND gate Ladder Implementation:

Use **normally open contacts in series**.

This is saying:

 

*"Only if A **AND** B are both TRUE, then turn ON the output."*

If either A or B is FALSE, current stops flowing — just like if one switch in a series circuit is off.


🔑 OR gate Ladder Implementation:

Use **normally open contacts in parallel**.

This is saying:

*"If A **OR** B is TRUE, then turn ON the output."*

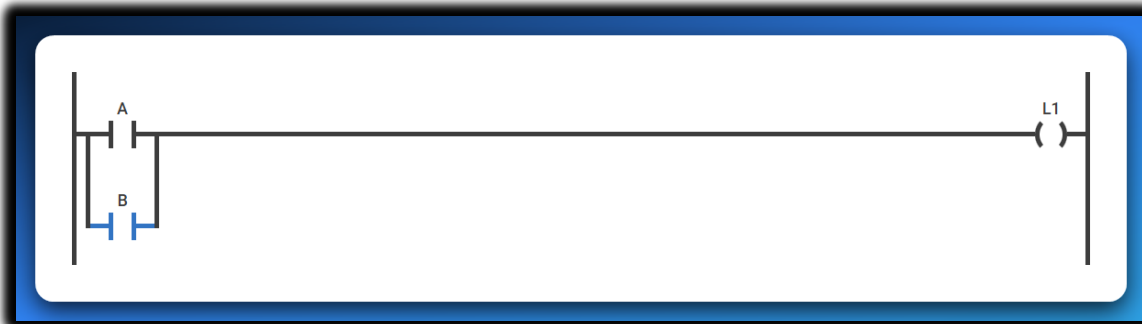As long as at least one of them is ON, the rung is complete and current flows to the output.



If **A is TRUE** (and B is FALSE), the path through A "closes," allowing logical power to flow to the output.

If **B is TRUE** (and A is FALSE), the path through B "closes," allowing logical power to flow to the output.

If **both A and B are TRUE**, both paths "close," and logical power still flows to the output.

Only if **both A and B are FALSE** will both paths remain "open," stopping the logical power flow and keeping the output OFF.

Key Concept: Contacts Are Logic Conditions

In Ladder Logic, your contacts (—| |—) aren't checking voltage directly — they're checking **bit states** in memory.

- A contact in a rung is **like a mini IF-statement**.
- When you place them **in series**, it means “all must be true” (AND).
- When you place them **in parallel**, it means “any can be true” (OR).

And these logic structures determine whether **your output coils (—()—)** get energized or not.

Analogy Time:

- Think of series logic like **security clearance**:
“You need both a keycard **and** a password to enter.”
- Think of parallel logic like **alarm triggers**:
“If **any** of the sensors trip, sound the alarm.”

Summary:


- **AND Logic = Series contacts** → All must be TRUE.
 - **OR Logic = Parallel contacts** → At least one must be TRUE.
 - No separate gate components — it's all about **how you arrange your contacts** in the rung.
-

🔑 Normally Open (NO) Contact – The “Push-to-Start”

Think of a normally open contact like a simple doorbell button.

- **Default (not pressed):** The internal path is open. No current flows. In PLC terms, the memory bit is FALSE (0).
- **When pressed:** The path closes. Electricity flows. In PLC terms, the bit flips to TRUE (1), and logical power can now travel through that rung.

 ✅ **Analogy:** Press button → bridge closes → current flows → light turns on.




🛡️ Normally Closed (NC) Contact – The “Safety Gate”

Now flip the logic. A normally closed contact is like a safety gate that’s already allowing current through until you interfere.

- **Default (not pressed):** The path is closed. Electricity flows. In PLC terms, the memory bit is TRUE (1).
- **When pressed:** The path opens. Current stops. In PLC terms, the bit reads FALSE (0), blocking logical power on that rung.

 ✅ **Analogy:** Press button → bridge opens → no current → light stays off.






💡 **Bottom line:**



NO let's power through *when active*. NC stops power *when active*.




Together, they're the Lego blocks of ladder logic—defining exactly when your rungs conduct or block logical “power.”

 
Simple, powerful, and everywhere in your PLC world.



 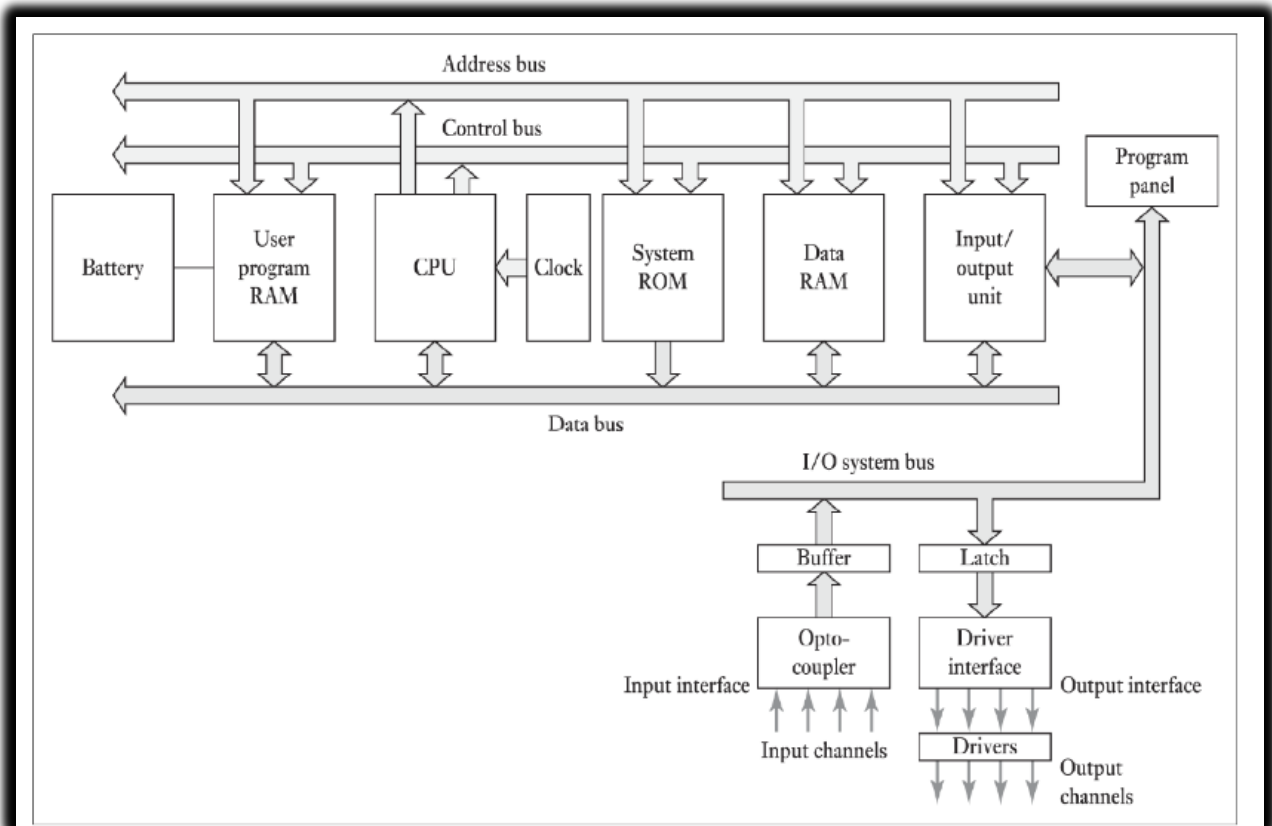


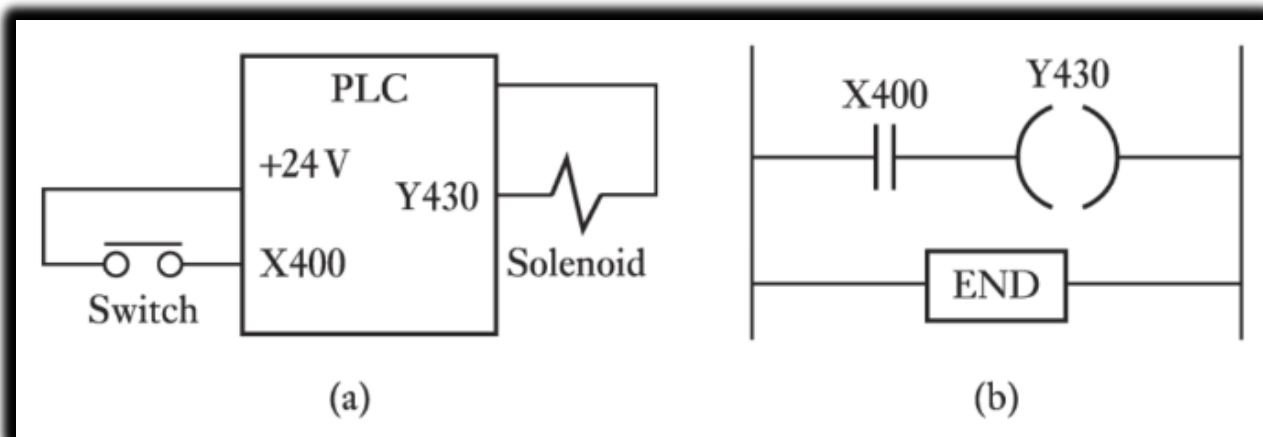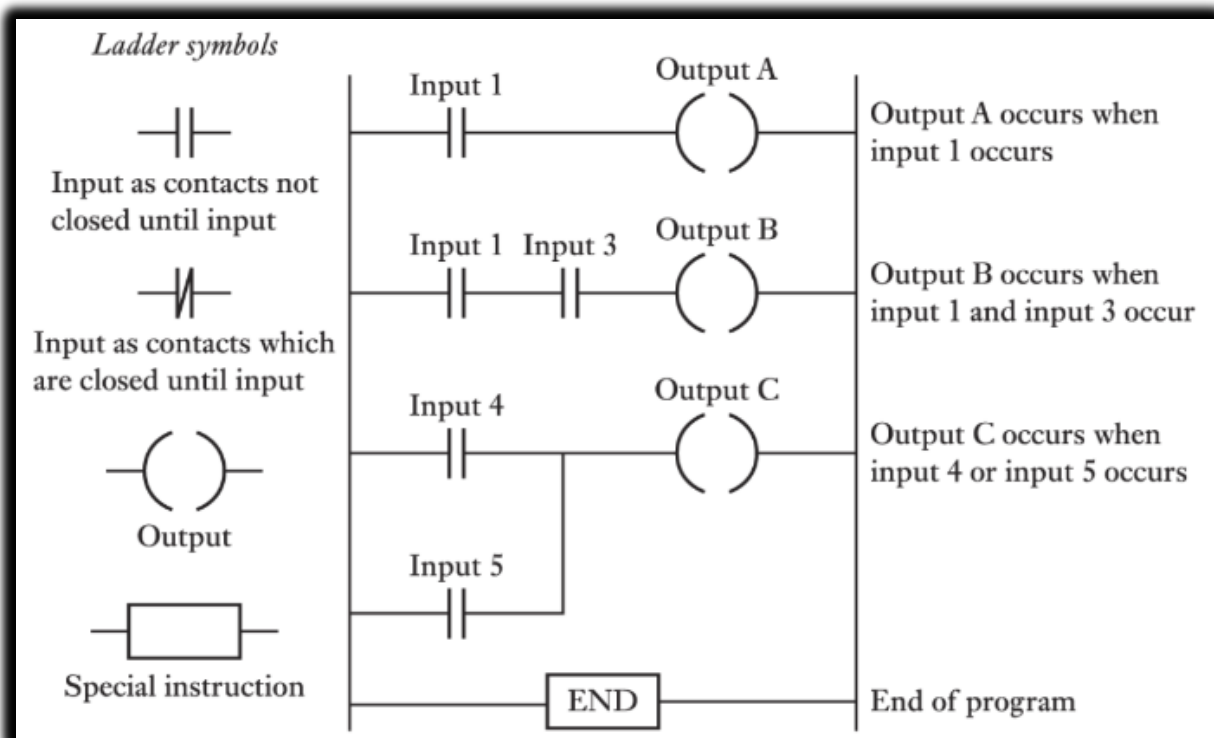

   


 


IEC 1131-3	Mitsubishi	OMRON	Siemens	Operation	Ladder diagram
LD	LD	LD	A	Load operand into result register	Start a rung with open contacts
LDN	LDI	LD NOT	AN	Load negative operand into result register	Start a rung with closed contacts
AND	AND	AND	A	Boolean AND	A series element with open contacts
ANDN	ANI	AND NOT	AN	Boolean AND with negative operand	A series element with closed contacts
OR	OR	OR	O	Boolean OR	A parallel element with open contacts
ORN	ORI	OR NOT	ON	Boolean OR with negative operand	A parallel element with closed contacts
ST	OUT	OUT	=	Store result register into operand	An output from a rung

 

 
LD X400 (*Input at address X400*)
AND X401 (*AND input at address X401*)
OUT Y430 (*Output to address Y430*)



 
LD X400 (*Input at address X400*)
OR X401 (*OR input at address X401*)
OUT Y430 (*Output to address Y430*)



 LDI X400 (*NOT input at address X400*)
ANI X401 (*AND NOT input at address X401*)
OUT Y430 (*Output to address Y430*)




 LDI X400 (*NOT input at address X400*)
ORI X401 (*OR NOT input at address X401*)
OUT Y430 (*Output to address Y430*)



(a)

 LD X400 (*Load input at address X400*)
ANI X401 (*AND NOT input at address X401*)
LDI X400 (*Load NOT input at address X401*)
AND X401 (*AND input at address X401*)
ORB
OUT Y430 (*Output to address Y430*)



(b)

A((*Load the bracketed term*)
A I0.0 (*Load input at address I0.1*)
AN I0.1 (*AND input at address I0.1*)
)
O((*OR the bracketed term*)
AN I0.0 (*Load NOT input at address I0.0*)
A I0.1 (*AND input at address I0.1*)
)
= Q2.0 (*Output to address Q2.0*)

