

LADDER LOGIC 2

🤖 Chapter 5-2: Basic Instructions in Ladder Logic

Boolean Logic and the DNA of Control

Now that you know what Ladder Logic looks like, it's time to understand **how it actually decides things**. And that takes us straight into **Boolean logic** — the bedrock of all decision-making in PLCs.


Don't worry, this isn't Digital Systems 101 — we're not breaking out Karnaugh maps or Boolean algebra proofs. We're just gonna look at the essentials: **AND** and **OR** logic.

❏ Boolean Logic in Plain Language

PLC logic is built on simple True/False decisions — like light switches:

- **TRUE (1)** → There's voltage or a condition is satisfied
- **FALSE (0)** → No voltage or the condition isn't satisfied

 
From this binary setup, we build logic gates. In Ladder Logic, these gates are **not separate components** — they're created through **how you arrange your rungs and contacts**.



The Gates — Series Logic


🔑 AND gate Ladder Implementation:

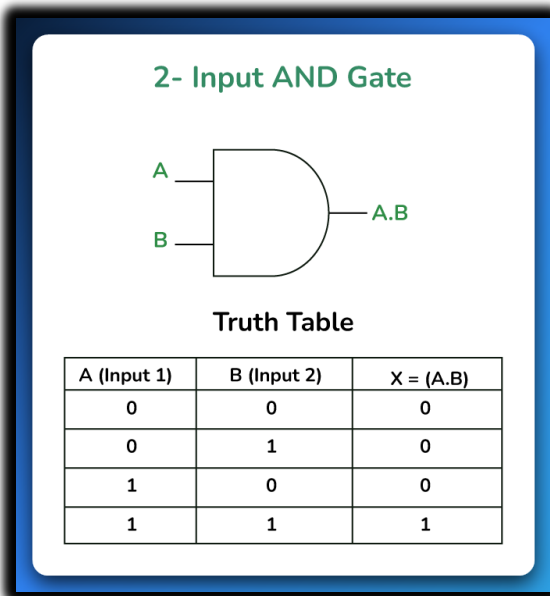AND operations are analogous to **multiplication**.



Use **normally open contacts** in series.

This is saying:

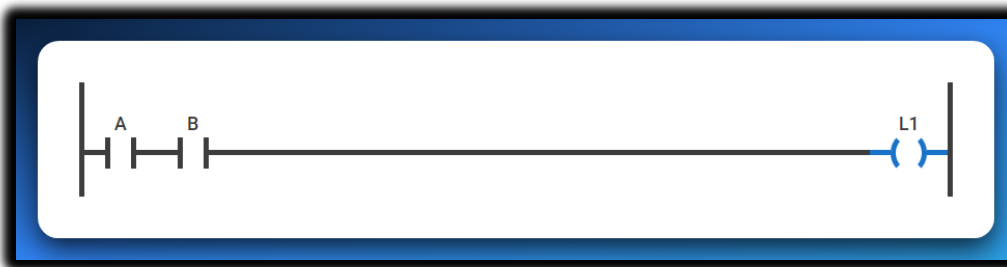

*"Only if A **AND** B are both TRUE, then turn ON the output."*


If either A or B is FALSE, current stops flowing — just like if one switch in a series circuit is off.

$$A \cdot B = X$$

OR gate Ladder Implementation:

Use **normally open contacts in parallel**.

 
OR operations are comparable to **addition**.



This is saying:

*"If A **OR** B is TRUE, then turn ON the output."*

 As long as at least one of them is ON, the rung is complete and current flows to the output.




If **A is TRUE** (and B is FALSE), the path through A "closes," allowing logical power to flow to the output.

If **B is TRUE** (and A is FALSE), the path through B "closes," allowing logical power to flow to the output.

If **both A and B are TRUE**, both paths "close," and logical power still flows to the output.

 
Only if **both A and B are FALSE** will both paths remain "open," stopping the logical power flow and keeping the output OFF.



🔑 NOT Gate Ladder Implementation:

Use a **normally closed (NC)** contact in series.
NOT operations are comparable to logical inversion.

Truth Table:

 

In short, Q is the opposite of A.

A NOT gate can only have one input. And its truth table is pretty simple since there are only two possible states; the input being HIGH (or “1”) or the input being LOW (or “0”).


This is saying:

“If A is NOT TRUE, then turn ON the output.”

As long as the input is **OFF (FALSE)**, the NC contact remains closed, allowing current (logical power) to flow to the output.

If the input becomes **ON (TRUE)**, the NC contact opens, breaking the circuit and stopping the output.

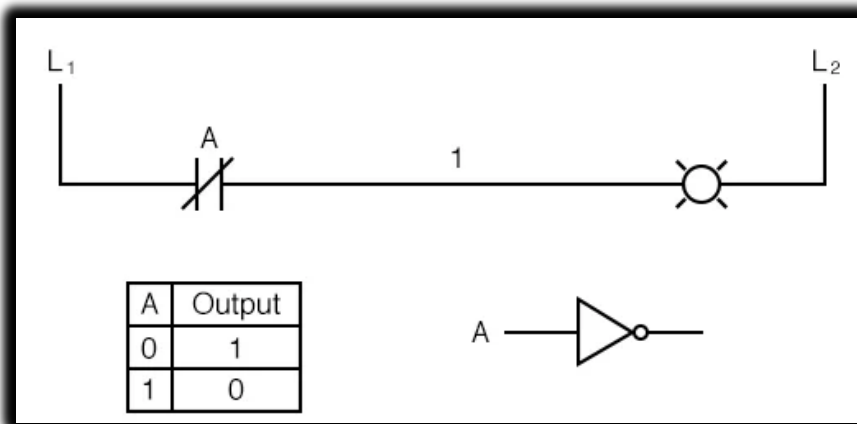In ladder form, you simply place an NC contact in front of the coil:




What it does: A NOT gate flips the input - if something is ON, it makes the output OFF, and vice versa.


How to build it in ladder logic: Use a Normally Closed (NC) contact --|/|--

- When input A is OFF → NC contact is closed → power flows → output turns ON
- When input A is ON → NC contact opens → no power flows → output turns OFF

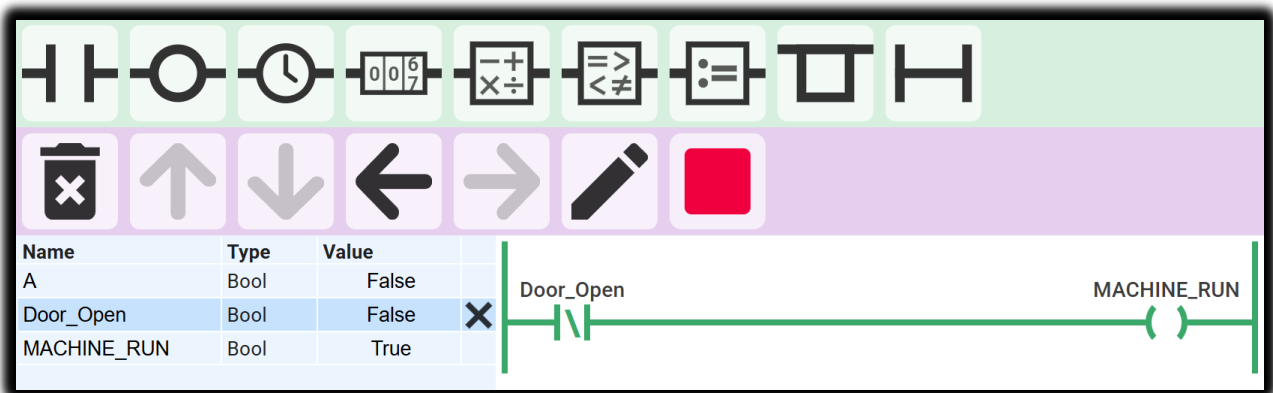Real-world example: Safety interlock on a machine door:



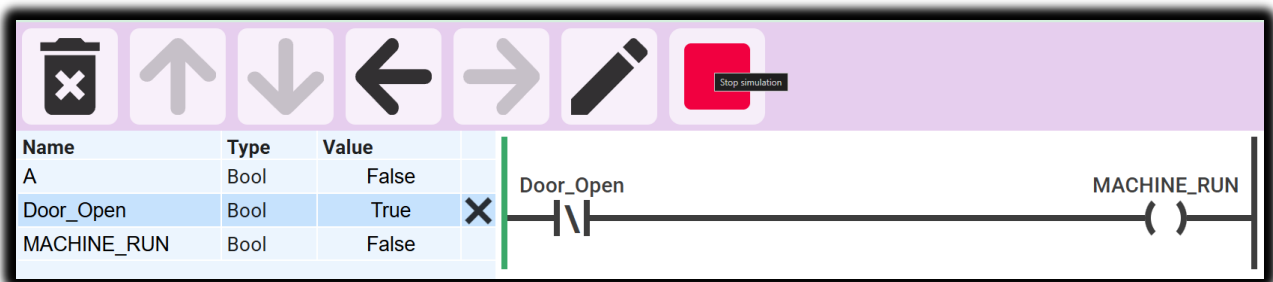Door is closed (DOOR_OPEN = 0 / False / NOT gate active) → machine can run (output = 1)





Door is open (DOOR_OPEN = 1 / True) → machine stops (output = 0)

In plain English: "Run the machine only when the door is NOT open." The NC contact automatically inverts the door sensor signal - when the door opens, it immediately cuts power to the machine.

This is the most basic safety logic you'll see everywhere in industrial automation.

🔑 XOR gate Ladder Implementation:

 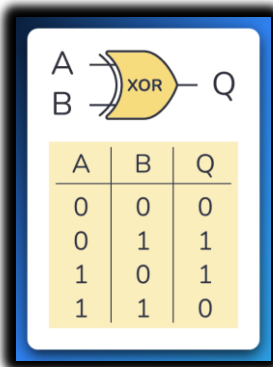

Use a combination of normally open (NO) and normally closed (NC) contacts.
This represents the logic: **"If A OR B is TRUE, but not both, then turn ON the output."**

How it works:

- **If A is TRUE and B is FALSE:**
The path through A (NO) and B (NC) closes → Output turns ON.
- **If B is TRUE and A is FALSE:**
The path through B (NO) and A (NC) closes → Output turns ON.
- **If both A and B are TRUE:**
Both paths are blocked because NC contacts open → Output stays OFF.
- **If both A and B are FALSE:**
Neither NO contact allows current → Output stays OFF.

✅ **Summary:** Output is ON **only when A or B is TRUE**, but **not both at the same time** — exactly what XOR logic means.

$$(A \cdot \bar{B}) + (\bar{A} \cdot B) = X$$

💡 Key Concept: Contacts Are Logic Conditions

In Ladder Logic, your contacts (—| |—) aren't checking voltage directly — they're checking **bit states** in memory.

- A contact in a rung is **like a mini IF-statement**.
- When you place them **in series**, it means “all must be true” (AND).
- When you place them **in parallel**, it means “any can be true” (OR).

And these logic structures determine whether **your output coils (—()—)** get energized or not.

🧠 Analogy Time:

- Think of series logic like **security clearance**:
“You need both a keycard **and** a password to enter.”
- Think of parallel logic like **alarm triggers**:
“*If **any** of the sensors trip, sound the alarm.*”

📌 Summary:

- **AND Logic = Series contacts** → All must be TRUE.
- **OR Logic = Parallel contacts** → At least one must be TRUE.
- No separate gate components — it's all about **how you arrange your contacts** in the rung.


The contacts

🔑 Normally Open (NO) Contact – The “Push-to-Start”

Think of a normally open contact like a simple doorbell button.

- **Default (not pressed):** The internal path is open. No current flows. In PLC terms, the memory bit is FALSE (0).
- **When pressed:** The path closes. Electricity flows. In PLC terms, the bit flips to TRUE (1), and logical power can now travel through that rung.

 ✅ **Analogy:** Press button → bridge closes → current flows → light turns on.




🛡️ Normally Closed (NC) Contact – The “Safety Gate”

Now flip the logic. A normally closed contact is like a safety gate that’s already allowing current through until you interfere.

- **Default (not pressed):** The path is closed. Electricity flows. In PLC terms, the memory bit is TRUE (1).
- **When pressed:** The path opens. Current stops. In PLC terms, the bit reads FALSE (0), blocking logical power on that rung.

 ✅ **Analogy:** Press button → bridge opens → no current → light stays off.




✨ Positive Transition-Sensing Contact ---|P|---

What it does: ☒ Fires **only for one scan** when your variable flips from FALSE → TRUE
☒ Think of it as a **one-shot rising edge detector** ☒ It only passes power if the left input is already TRUE at that moment

Real-world examples:

- **Start button:** Press to start a machine → you want it to start once, not keep trying to start every scan while held down.
- **Part counter:** When a sensor first detects a part → increment counter once, not continuously while the part passes by.
- **Door opening:** When a door switch goes from closed to open → log one "door opened" event, not hundreds while it stays open.
- **Emergency reset:** After fixing an alarm → acknowledge it once when the reset button is pressed, not repeatedly.

 Why it's essential: Without this, holding a button would flood your system with repeated commands every scan cycle (potentially thousands of times per second), causing chaos in counters, alarms, and sequences.



✨ Negative Transition-Sensing Contact ---|N|---

What it does: ✓ Fires **only for one scan** when your variable flips from TRUE → FALSE

✓ A **one-shot falling edge detector** ✓ Left input must be TRUE at that moment too

Real-world examples:

- **Conveyor control:** When a box leaves the sensor → start the next conveyor section once, not continuously while the sensor is empty
- **Safety logging:** When an emergency stop is released → log one "system restored" event at the exact moment of release
- **Production tracking:** When a part exits the work station → trigger completion counter once as it leaves, not while the station stays empty
- **Door security:** When a door closes → send one "door secured" signal to the alarm system, not constant signals while it stays closed
- **Process completion:** When a tank empties (level sensor goes FALSE) → start the refill cycle once at that instant

Why it's crucial: This catches the exact moment something stops or leaves, preventing your system from missing the transition or triggering multiple times. Perfect for "cleanup" actions that should happen right when something ends.



⚡ OTE (Output Energize) or Output Coil


Think of OTE as the "**result**" of your ladder logic rung. It's what actually happens when all your conditions are met.

Simple analogy: You know how a regular light switch works? You flip it up → light turns on. You flip it down → light turns off. OTE is exactly like that light bulb, but instead of a physical switch, it's controlled by the logic you build.

How it really works: Every time the PLC scans your program (thousands of times per second), it checks: "Are all the conditions on this rung TRUE right now?"

- If YES → OTE energizes (turns ON)
- If NO → OTE de-energizes (turns OFF)

 Real-world example: Imagine an automatic parking garage gate:



- Car sensor detects a vehicle AND payment was received AND gate isn't broken → gate opens
- Missing any one condition (no car, no payment, gate broken) → gate stays closed
- The gate follows these conditions in real-time - if payment expires while the car is there, gate closes immediately

Key point: OTE has zero memory. It's like a faithful dog - it does exactly what you tell it, when you tell it, every single scan. No thinking, no remembering yesterday, just pure obedience to your current logic.

The OTE (Open_Gate) is like the "DO IT!" command at the end of the line. When everything to the left of Open_Gate is TRUE (like, all the green lights are on and the vibes are right), then Open_Gate gets powered up, and it stays on as long as those conditions are met.

🚪 Latch (OTL) and Unlatch (OTU)

OTL (Output Latch) - The Memory Keeper


In simple terms: OTL is like a **sticky switch** - once you turn it ON, it STAYS on until something specifically turns it OFF.

How it's different from OTE:

- **OTE:** Acts like a regular light switch - follows your logic constantly
- **OTL:** Acts like a **hotel room keycard** - once activated, it remembers and stays active

How OTL works: When the rung logic goes TRUE (even for just one scan), OTL sets the output to ON and then **remembers** that state. Even if the rung logic goes back to FALSE, the output STAYS ON.

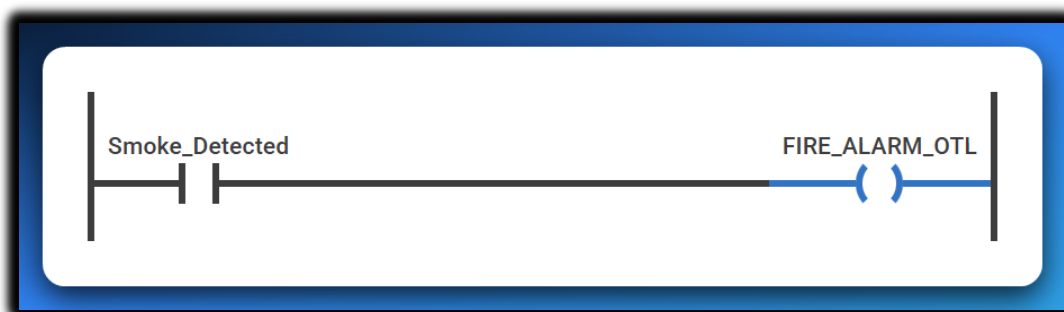Real-world example: Emergency alarm system (we'll unlatch it next):



- Smoke sensor triggers for 2 seconds → alarm turns ON
- Smoke clears (sensor goes FALSE) → alarm STAYS ON (latched)
- Alarm keeps blaring until someone manually resets it with an OTU instruction

Why use latching? Perfect for situations where you need something to **stay active** even after the trigger condition disappears:



- Emergency alarms that need manual reset
- Equipment that should stay running once started
- Status flags that mark "something happened" until cleared

Key point: OTL has **permanent memory** - it's like writing with a pen instead of pencil. Once it's set, only an OTU (Output Unlatch) can erase it.

OTU (Output Unlatch) - The Reset Button

In simple terms: OTU is the **eraser** for latched outputs. It specifically turns OFF outputs that were set by OTL instructions.

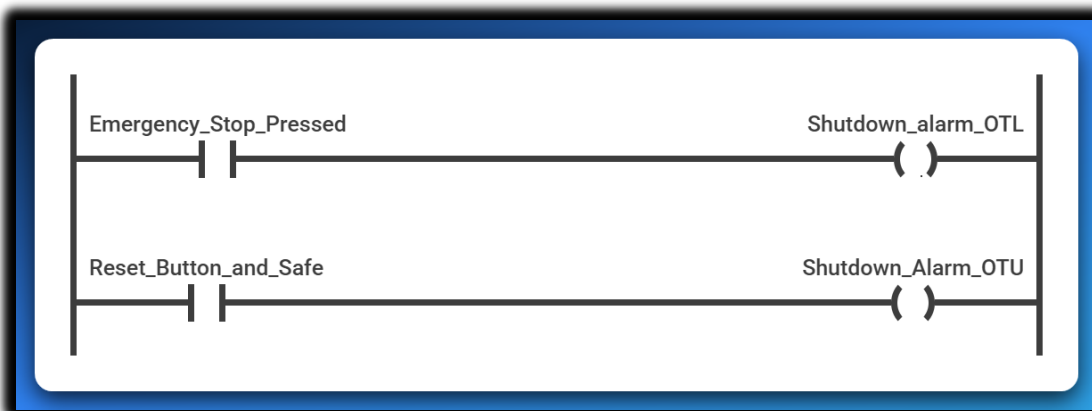 How it works: When the rung logic goes TRUE, OTU forces the specified output to turn OFF and clears its "memory." It's like hitting a reset button. The OTL/OTU partnership:



- Emergency button pressed → alarm latches ON and STAYS on
- Even if emergency button is released → alarm keeps sounding
- Only when technician presses reset AND system is safe → OTU turns alarm OFF

Key differences:

- **OTL:** Sets something ON permanently (until reset)
- **OTU:** Sets something OFF permanently (until latched again)
- **OTE:** Just follows current logic (no memory)

Important: OTU only affects outputs that were previously latched with OTL. It's like having a specific key that only works on doors that were locked with a matching lock.


💡 **Bottom line:**

NO let's power through *when active*. NC stops power *when active*.

Together, they're the Lego blocks of ladder logic—defining exactly when your rungs conduct or block logical “power.”

Simple, powerful, and everywhere in your PLC world.

A PLC.

 

By now we're good to go forward with this topic.


LADDER LOGIC PART 3

Elements of ladder logic

- **Rails** – Vertical lines that carry electrical power to the control circuit.
- **Rungs** – Horizontal lines where the logic is built; they contain inputs, outputs, and branches.
- **Branches** – Parallel paths on a rung that allow multiple input conditions.
- **Inputs** – Devices like switches or sensors that control the logic flow.
- **Outputs** – Devices like motors or lights activated by the logic.
- **Timer** – Delays actions for a set time (e.g., turn on a light after 5 seconds).
- **Counter** – Counts events or cycles and triggers actions after a set number.

I see a small naming confusion I have always had.

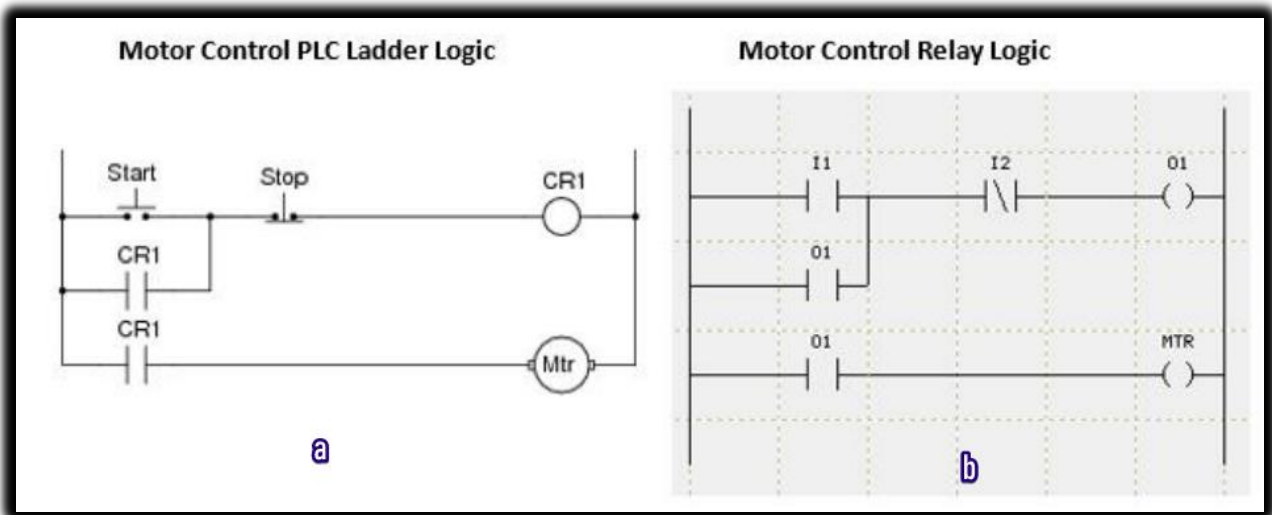In my school, we used “Ladder Logic” to refer to the programs we were drawing.



So, I had this conflict calling the **image b** ladder logic.


Now am seeing it being called **relay logic**.

- **Diagram 'a' (Motor Control PLC Ladder Logic):** This is a **program** that runs inside a PLC. It's software.

- **Diagram 'b' (Motor Control Relay Logic):** This is a **wiring diagram** for physical electrical components (relays, switches, motor). It's hardware.


Some Practice

$$Y = (X1 + X2)X3$$

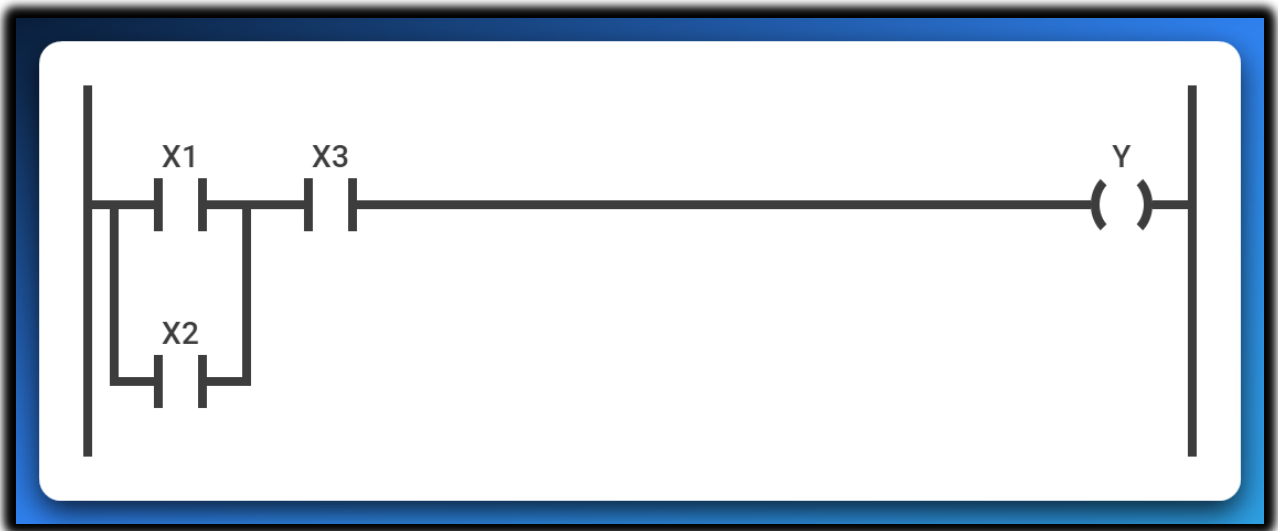



Read it using the AND, OR gates.



$$Y = (X1 + X2)(X3 + X4)$$


 





You could attach the midpoint lines as one, or separate them as above.


$$Y = (X1X2) + X3$$

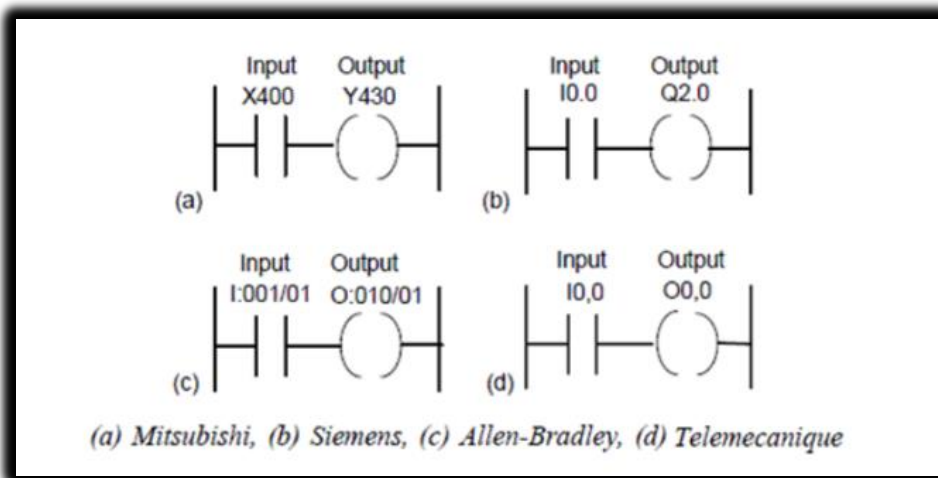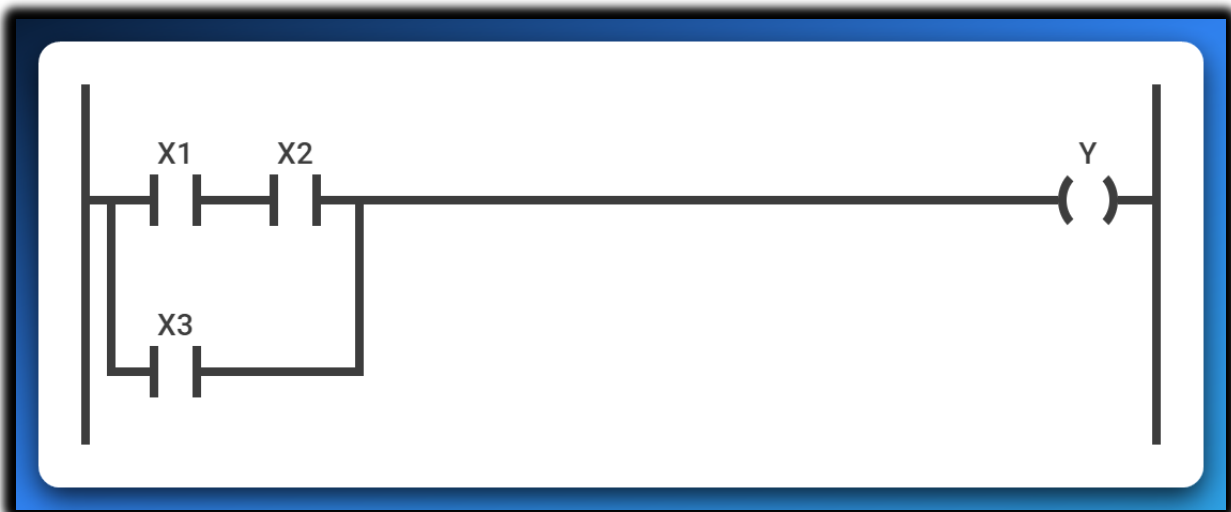

 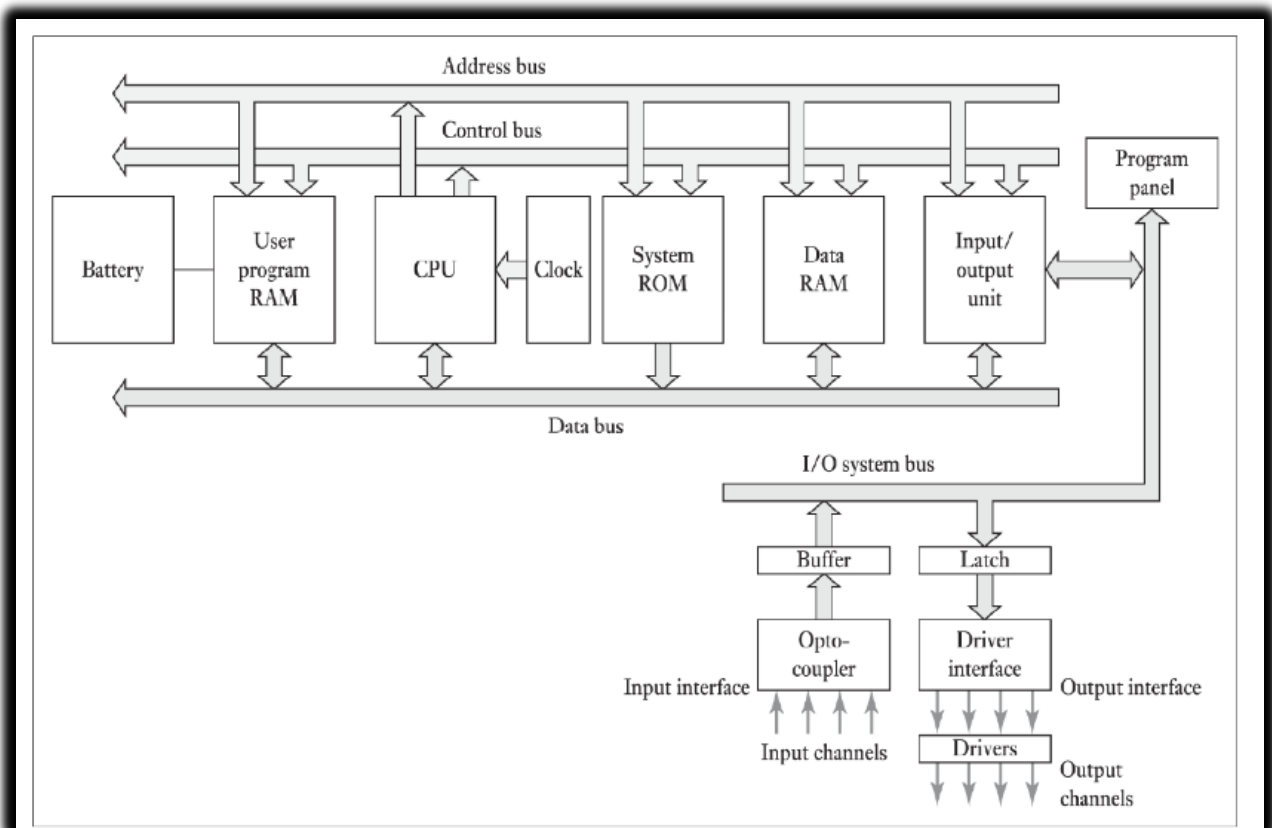


  

   


 


IEC 1131-3	Mitsubishi	OMRON	Siemens	Operation	Ladder diagram
LD	LD	LD	A	Load operand into result register	Start a rung with open contacts
LDN	LDI	LD NOT	AN	Load negative operand into result register	Start a rung with closed contacts
AND	AND	AND	A	Boolean AND	A series element with open contacts
ANDN	ANI	AND NOT	AN	Boolean AND with negative operand	A series element with closed contacts
OR	OR	OR	O	Boolean OR	A parallel element with open contacts
ORN	ORI	OR NOT	ON	Boolean OR with negative operand	A parallel element with closed contacts
ST	OUT	OUT	=	Store result register into operand	An output from a rung

 

 
LD X400 (*Input at address X400*)
 AND X401 (*AND input at address X401*)
 OUT Y430 (*Output to address Y430*)



 
LD X400 (*Input at address X400*)
 OR X401 (*OR input at address X401*)
 OUT Y430 (*Output to address Y430*)



 LDI X400 (*NOT input at address X400*)
 ANI X401 (*AND NOT input at address X401*)
 OUT Y430 (*Output to address Y430*)




 LDI X400 (*NOT input at address X400*)
 ORI X401 (*OR NOT input at address X401*)
 OUT Y430 (*Output to address Y430*)



(a)

 LD X400 (*Load input at address X400*)
 ANI X401 (*AND NOT input at address X401*)
 LDI X400 (*Load NOT input at address X401*)
 AND X401 (*AND input at address X401*)
 ORB
 OUT Y430 (*Output to address Y430*)



(b)

A((*Load the bracketed term*)
 A I0.0 (*Load input at address I0.1*)
 AN I0.1 (*AND input at address I0.1*)
)
 O((*OR the bracketed term*)
 AN I0.0 (*Load NOT input at address I0.0*)
 A I0.1 (*AND input at address I0.1*)
)
 = Q2.0 (*Output to address Q2.0*)

